

SYSTEM MODELLING AND SYNTHESIS WITH HDL

DTEK0078

2022 Lecture 8



UNIVERSITY
OF TURKU



Our research website: <https://tiers.utu.fi/>



Finite State Machines



UNIVERSITY
OF TURKU



Mealy and Moore

Moore machine's outputs are a function of the present state only

Mealy machine's outputs are a function of the present state and present inputs



Mealy and Moore

Can be functionally equivalent

Mealy usually requires smaller number of states

Mealy reacts one clock cycle sooner than Moore

Moore does not have a combinational path from input to output

Finite State Machine

- A finite state machine (FSM) is an abstraction of a sequential circuit whose possible internal states are enumerated by the designer
- The FSM is always in exactly one state (called its current state) and can transition to a different state in response to an event
- To design an FSM, we must specify its
 - states, input signals, output signals, next-state function, and output function
- The outputs of an FSM may depend on its current state and current inputs

Finite State Machine

- Can be implemented as single process or two process ways
 - single-process FSM: all the blocks are implemented in the same process statement
 - two-process FSM: the most common division is to code the state register as a clocked process and the next state and output logic blocks as a combinational process

```

architecture single_proc of turnstile_fsm is
begin
  process (clock, reset)
    type state_type is (locked, unlocked);
    variable state: state_type;
  begin
    -- Single process for state register,
    -- next-state logic, and output logic:
    if reset then
      state := locked;
      lock <= '1';
    elsif rising_edge(clock) then
      case state is
        when locked =>
          if ticket_accepted then
            lock <= '0';
            state := unlocked;
          else
            lock <= '1';
            state := locked;
          end if;
        when unlocked =>
          if pushed_through then
            lock <= '1';
            state := locked;
          else
            lock <= '0';
            state := unlocked;
          end if;
        end case;
      end if;
    end process;
  end architecture;

```

```

architecture two_proc of turnstile_fsm is
  type state_type is (locked, unlocked);
  signal current_state, next_state:
    state_type;
begin
  -- State register:
  process (clock, reset) begin
    if reset then
      current_state <= locked;
    elsif rising_edge(clock) then
      current_state <= next_state;
    end if;
  end process;

  -- Next-state and output logic:
  process (all) begin
    case current_state is
      when locked =>
        if ticket_accepted then
          lock <= '0';
          next_state <= unlocked;
        else
          lock <= '1';
          next_state <= locked;
        end if;
      when unlocked =>
        if pushed_through then
          lock <= '1';
          next_state <= locked;
        else
          lock <= '0';
          next_state <= unlocked;
        end if;
      end case;
    end process;
  end architecture;

```

Single

- + entirely encapsulated implementation within the process
- + a single object to keep the state
- + no risk of accidental latches
- all outputs are registered by default
- may become too complicated

```
architecture single_proc of turnstile_fsm is
begin
```

```
  process (clock, reset)
```

```
    type state_type is (locked, unlocked);
```

```
    variable state: state_type;
```

```
  begin
```

```
    -- Single process for state register,  
    -- next-state logic, and output logic:
```

```
    if reset then
```

```
      state := locked;
```

```
      lock <= '1';
```

```
    elsif rising_edge(clock) then
```

```
      case state is
```

```
        when locked =>
```

```
          if ticket_accepted then
```

```
            lock <= '0';
```

```
            state := unlocked;
```

```
          else
```

```
            lock <= '1';
```

```
            state := locked;
```

```
          end if;
```

```
        when unlocked =>
```

```
          if pushed_through then
```

```
            lock <= '1';
```

```
            state := locked;
```

```
          else
```

```
            lock <= '0';
```

```
            state := unlocked;
```

```
          end if;
```

```
architecture two_proc of turnstile_fsm is
```

```
  type state_type is (locked, unlocked);
```

```
  signal current_state, next_state:
```

```
    state_type;
```

```
begin
```

```
  -- State register:
```

```
  process (clock, reset) begin
```

```
    if reset then
```

```
      current_state <= locked;
```

```
    elsif rising_edge(clock) then
```

```
      current_state <= next_state;
```

```
    end if;
```

```
  end process;
```

```
  -- Next-state and output logic:
```

```
  process (all) begin
```

```
    case current_state is
```

```
      when locked =>
```

```
        if ticket_accepted then
```

```
          lock <= '0';
```

```
          next_state <= unlocked;
```

```
        else
```

```
          lock <= '1';
```

```
          next_state <= locked;
```

```
        end if;
```

```
      when unlocked =>
```

```
        if pushed_through then
```

```
          lock <= '1';
```


```
          next_state <= locked;
```

Two

- + Output are registered or not
- + Each process has a clear task
- Bad design leads unwanted latches
- may become too complicated

Finite State Machine

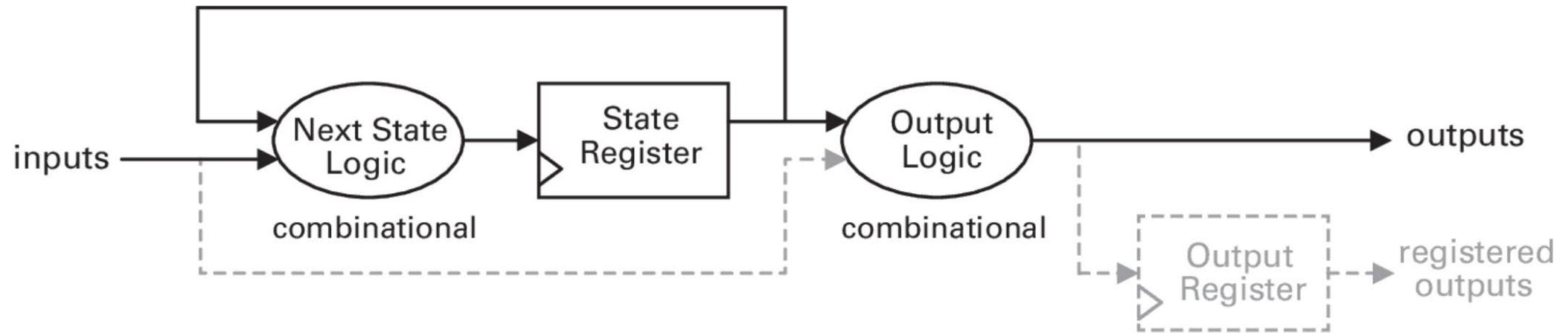- An FSM can be implemented as a synchronous digital circuit using a register to keep its current state, and combinational logic to implement the next-state and output functions



VHDL outline for Moore Machine

```
type statemachine is (S0, S1, ... , SX);
signal state: statemachine;

Moore: process(clock, reset)
begin
    if (reset = '1') then state <= S0;
    elsif (clock = '1' and clock'event) then
        case state is
            when S0 =>
                if input = '1' then state <= S1;
                else state <= S0;
                end if;
            when S1 =>
                ...
            end case;
        end if;
    end process;

output <= '1' when state = SX else '0';
```

VHDL outline for Mealy Machine

```
type statemachine is (S0, S1, ... , SX);
signal state: statemachine;

Mealy: process(clock, reset)
begin
    if (reset = '1') then state <= S0;
    elsif (clock = '1' and clock'event) then
        case state is
            when S0 =>
                if input = '1' then state <= S1;
                else state <= S0;
                end if;
            when S1 =>
                ...
            end case;
        end if;
    end process;

    output <= '1' when (state = SX-1 and input = '0|1') else '0';
```

Generics




```
entity_declaration ::=
    entity identifier is
        [ generic ( generic_interface_list ) ; ]
        [ port ( port_interface_list ) ; ]
    end [ entity ] [ entity_simple_name ] ;

generic_interface_list ::=
[ constant ] identifier_list : [ in ] subtype_indication [ := static_expression ]
{ [ constant ] identifier_list : [ in ] subtype_indication [ := static_expression ] }
```

Generics


- Generics allow a design to be described so that its structure can be altered easily during the instantiation of the module

Generic Example

- Generics are visible in the entity in which it is declared as well as in the corresponding architecture body

```
entity half_adder is
  generic (Tpd: time := 10 ns)
  port( x,y: in std_logic;
        sum, carry: out std_logic);
end half_adder;

 architecture myadder of half_adder is
begin
  sum <= x xor y after Tpd;
  carry <= x and y after Tpd;
end myadder;
```



Up Counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Counte3 is
port( clk   : in  std_logic;
      reset: in  std_logic;
      count: out std_logic_vector(3 downto 0));
end Counte3;

architecture behavioural of Counte3 is
    signal counting: std_logic_vector(3 downto 0);
begin
    process (clk,reset)
    begin
        if reset = '0' then
            counting <= "0000";
        elsif (rising_edge(clk)) then
            counting <= counting + 1;
        end if;
    end process;
    count <= counting;
end behavioural;
```

Up Counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Counte3 is
generic( w: natural := 4)
port( clk:   in std_logic;
      reset: in std_logic;
      count: out std_logic_vector(w-1 downto 0));
end Counte3;

architecture behavioural of Counte3 is
  signal counting: std_logic_vector(w-1 downto 0);
begin
  process (clk,reset)
  begin
    if reset = '0' then
      counting <= (others => 0);
    elsif (rising_edge(clk)) then
      counting <= counting + 1;
    end if;
  end process;
  count <= counting;
end behavioural;
```


Port Mapping with Generics

```
entity Counte3 is
    generic( w: natural := 4)
    port( clk: in std_logic;
          reset: in std_logic;
          count: out std_logic_vector(w-1 downto 0));
end Counte3;
```

```
c1:    entity work.counter (behavioural)
        generic map (16)
        port map (m_clk, m_reset, m_count1);
```

```
c2:    entity work.counter (behavioural)
        generic map (12)
        port map (m_clk, m_reset, m_count2);
```

```
c3:    entity work.counter (behavioural)
        generic map (w => 16)
        port map (m_clk, m_reset, m_count3);
```

Port Mapping with Generics (VHDL-2008)

```
generic ( type T; constant init_val : T );  
signal v : T := init_val;
```

```
entity Counte3 is  
    generic( type data_type)  
    port( clk: in std_logic;  
          reset: in std_logic;  
          count: out data_type);  
end Counte3;
```

```
c1: entity work.counter (behavioural)  
    generic map (data_type => std_logic_vector(3 downto 0))  
    port map (m_clk, m_reset, m_count);
```

Port Mapping with Generics (VHDL-2008)

NOTE

- To use types in generics requires one to be careful!
- For example, arithmetic operators are not defined for all the available types

```
entity counte3 is
generic( type data_type )
port( . . .
      Dout : out
data_type);
architecture
. . .
Dout <= Dout + 1;
end architecture;
```



**UNIVERSITY
OF TURKU**